


More Complex Combinational Circuit Design using VHDL Programming

Presented by
Dr. Sudipta Basu Pal
CST & CSIT, UEM, Kolkata

Write a VHDL program to implement 2x4 Decoder using Case statement.

- Title: Implementing 2x4 Decoder using Case statement.
- Expression : $D_0 = X'Y'$; $D_1 = X'Y$; $D_2 = XY'$;
 $D_3 = XY$

Circuit Diagram :

 

Truth Table

| A_1 | A_0 | D_3 | D_2 | D_1 | D_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

Equations

$$D_0 = \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{A_1} \cdot A_0$$

$$D_2 = A_1 \cdot \overline{A_0}$$

$$D_3 = A_1 \cdot A_0$$

VHDL-CODE

```
library IEEE;
    use IEEE.std_logic_1164.all;
    use IEEE.std_logic_arith.all;
    use IEEE.std_logic_unsigned.all;

entity decod2to4_case is
port (
    sel : in std_logic_vector(1 downto 0);

    output : out std_logic_vector(3 downto 0));

end entity decod2to4_case ;
```

CODE-CONTINUED

```
architecture arc of decod2to4_case is
begin
    process (sel) is
        begin
            case sel is
                when "00" => output <= "0001";
                when "01" => output <= "0010";
                when "10" => output <= "0100";
                when others => output <= "1000";
            end case;
        end process;
    end architecture arc;
```


OUTPUT-WAVEFORM



Write a VHDL program to implement Priority Encoder using If-Else statement.

- Title : Implementing a Priority Encoder using If-Else statement.
- Expression : $O_0 = I_1 + I_3$; $O_1 = I_2 + I_3$

Circuit Diagram :

 

Truth Table :

| INPUTS | | | | OUTPUTS | |
|--------|----|----|----|---------|----|
| Y3 | Y2 | Y1 | Y0 | A1 | A0 |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

VHDL-CODE

```
library IEEE;
    use IEEE.std_logic_1164.all;
    use IEEE.std_logic_arith.all;
    use IEEE.std_logic_unsigned.all;


entity encod4to2_if is
port (
    input : in std_logic_vector(3 downto 0);

    output : out std_logic_vector(1 downto 0));

end entity encod4to2_if ;

architecture arc of encod4to2_if is
begin
    process (input) is
        begin
            if input = "0001" then output <= "00";
            elsif input = "0010" then output <= "01";
            elsif input = "0100" then output <= "10";
            elsif input = "1000" then output <= "11";
            else output <= "XX";
            end if;
        end process;
    end architecture arc;
```

OUTPUT-WAVEFORM

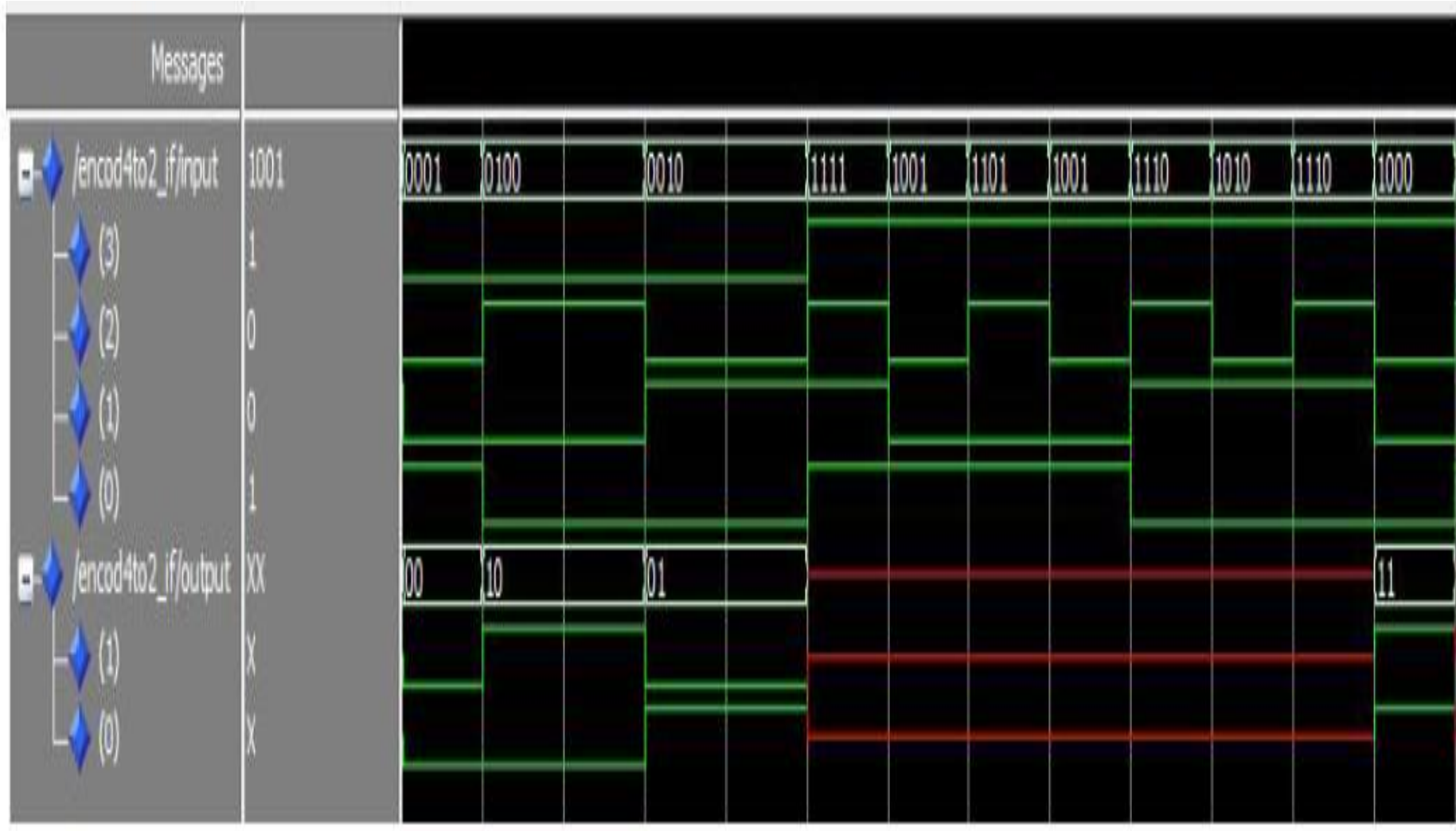


Sequential Circuits

- FLIP FLOP
- REGISTER
- COUNTER

Design a SR flip-flop using VHDL

Circuit-Diagram

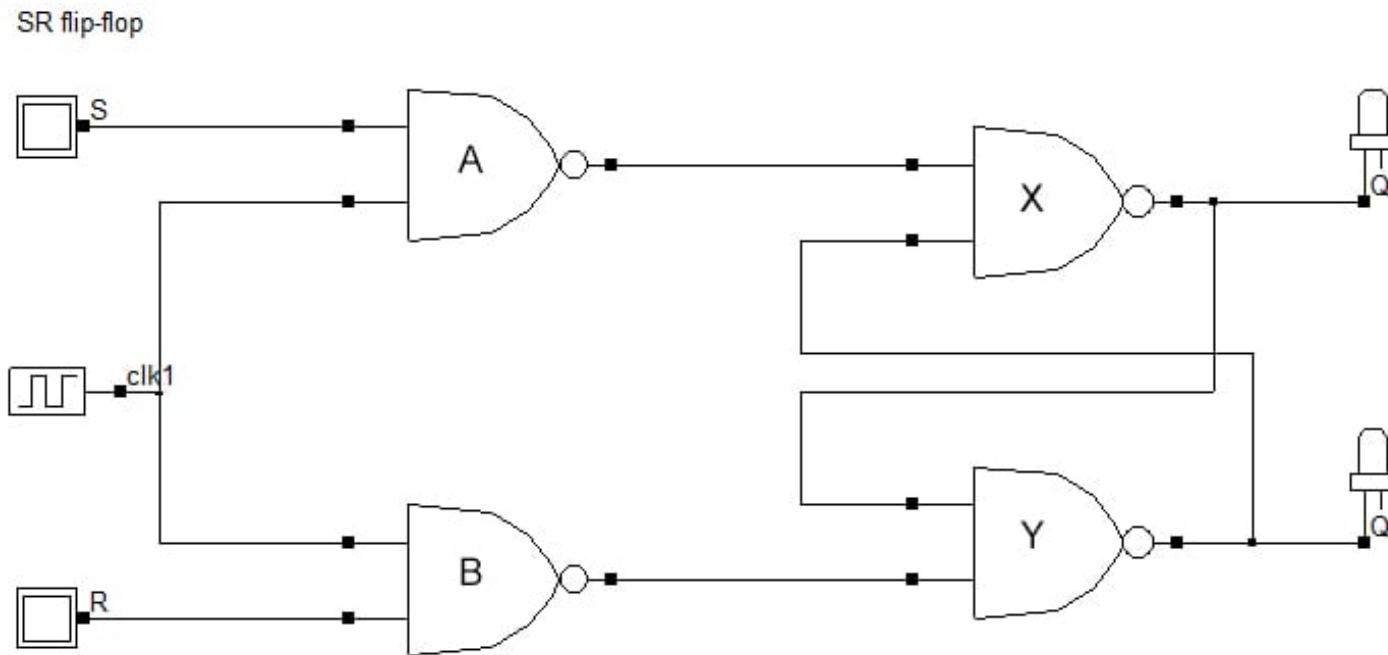

Truth table

| CLK | S | R | Q | Q' |
|-----|---|---|------------------|-------------------|
| 0 | x | x | Q _{prv} | Q' _{prv} |
| 1 | 0 | 0 | Q _{prv} | Q' _{prv} |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | — | — |

VHDL CODE

- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL;
- use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity SR_FLIPFLOP_SOURCE is
- Port (S,R,RST,CLK : in STD_LOGIC;
- Q,Qb : out STD_LOGIC);
- end SR_FLIPFLOP_SOURCE;

- architecture Behavioral of SR_FLIPFLOP_SOURCE is

- begin

- process (S,R,RST,CLK)
- Begin
- if (RST = '1') then
- Q <= '0';
- elsif (RISING_EDGE(CLK))then
- if (S /= R) then
- Q <= S;
- Qb <= R;
- elsif (S = '1' AND R = '1') then
- Q <= 'Z';
- Qb <= 'Z';
- end if;
- end if;
- end process;
- end Behavioral;

Waveform

