 


Assignment - 1

- 1) Write a VHDL program to implement all the AND gates using data flow.

Title :- Implementation of AND gate using data flow modelling.

Symbolic Diagram :-



Boolean Expression :- $[A \cdot B]$

Truth Table :-

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

VHDL Code :-

Library IEEE;

use IEEE.std_logic-1164.all;

entity AND_gate is

port (A: in std_logic;

B: in std_logic;

Y: out std_logic);

end AND_gate;


architecture andLogic of AND_gate is

begin

Y <= A AND B;

end andLogic;


Output Waveforms

 

2) Write a VHDL program to implement all OR Gate using data flow modelling.

Title :- Implementation of OR Gate using data flow modelling.

Symbolic Diagram :-

 

Boolean Expressions :- $(A + B)$

Truth Table :-

A	B	$Y = (A + B)$
0	0	0
0	1	1
1	0	1
1	1	1

VHDL Code :-

Library IEEE;

use IEEE.std_logic-1164.all;

entity OR-gate is

Port (A : in std_logic;
B : in std_logic;
Y : out std_logic;)


end OR-gate;

architecture OR-gateLogic of OR-gate is

begin
Y <= A AND B;
end andLogic;

Y <= A AND B;
end OR-gateLogic;

Output Waveform :-

 

3) Write a VHDL Programming to implement all NOT Gate using data flow modelling.

Title:- Implementation of NOT Gate using data flow modelling.

Symbolic Diagram :- 

Truth Table:-

A	A' = Y
0	1
1	0

VHDL Code:-

Library IEEE;

use IEEE.std_logic_1164.all;

entity NOT_gate is

Port (A: in std_logic;
Y: out std_logic);

end NOT_gate;


architecture NOTLogic of NOT_gate is

begin

Y <= NOT(A);

end NOTLogic;

Output Waveform

 

4) Write a VHDL programs to implement all NAND Gate using data flow modelling.

Title:- Implementation of NAND Gate using data flow modeling.

Boolean Expression:- $Y = \overline{A \cdot B}$

Symbolic Diagram:-




Truth Table:-

A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

VHDL Code:-

```
Library IEEE;
use IEEE_std_logic_1164.all;
entity NAND_gate is
    Port (A: in std_logic;
          B: in std_logic;
          Y: out std_logic);
end NAND_gate;
architecture NANDLogic of NAND_gate is
begin
    Y <= A NAND B;
end NANDLogic;
```

Output Waveform

 

5) Write a VHDL Program to implement all NOR Gate using data flow modeling.

Title:- Implementation of NOR gate using data flow modeling

Boolean Expression:- $Y = \overline{A + B}$

Symbolic Diagram:-




Truth Table:-

A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

VHDL Code:-

```
Library IEEE;
use IEEE - std - logic - 1164 all;
entity NORgate is
    Port ( A: in std - logic;
           B: in std - logic;
           Y: out std - logic);
end NORgate;
architecture NORLogic of NORgate is
begin
    Y <= A NOR B;
end NORLogic;
```


Output Waveform:-

 

- 6) Write a VHDL program to implement all XOR Gate using data flow modeling.

Title:- Implementation of XOR gate using data flow modeling

Boolean Expression:- $Y = A \oplus B$

Symbolic Diagram:- 

Truth Table :-


A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

VHDL CODE:-

```

Library IEEE;
use IEEE_std_logic_1164.all;
entity XORgate is
    port (A: in std_logic;
          B: in std_logic;
          Y: out std_logic);
end XORgate;
architecture XORLogic of XORgate is
begin
    Y <= A XOR B;
end XORLogic;
    
```

Output Waveform:-

 

7) Write a VHDL program to implement all XNOR Gate using data flow modeling.

Title:- Implementation of XNOR gate using data flow modeling.

Boolean Expression:- $Y \Rightarrow Y = \overline{A \oplus B}$

Symbolic Diagram:-



Truth Table:-

A	B	$Y = \overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

VHDL CODE:-

Library IEEE;

use IEEE_std_logic_1164.all;

entity XNORg is

Port (A: in std_logic;

B: in std_logic;

Y: out std_logic);

end XNORg;

architecture XNORLogic of XNORg is

begin

$Y \leq A \text{ XNOR } B;$

end XNORLogic;

Output Waveform:-

